

Introduction to Robotics

Lecture 1: Introduction

17. 9. 2018

ParaDiSe


What Are We Up To

Build an overview in the robotics field from A to Z.

- get familiar with a low-level hardware & learn to tackle hardware-related problems
 - simple (digital) electronics
 - screws, glue, hacksaw...
 - etc.
- learn to program bare-metal MCUs
- get familiar with basic sensors & actuators
- learn the high level theory
- fill the gap between the low level stuff and high level abstracted view on robotics

What Are We Not Up To

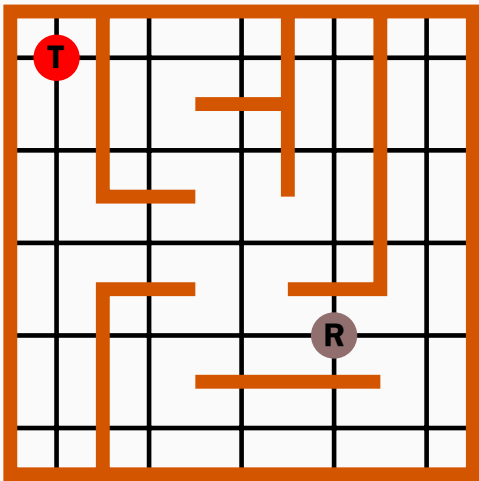- learn to produce industrial-grade robots
- getting tied to a specific platform
 - we will work with Atmel based 8-bit MCUs
 - but in theory we will cover other vendors and solutions
- learning advanced electronics & mechanics
 - no analog circuitry
 - no custom PCBs
 - no (sophisticated) custom mechanics



Build an autonomous robot which is able to:

- move in square grid based maze
 - using guide lines and
 - walls
- explore the maze and fulfil given tasks:
 - find a spot with given property
 - build a map and navigate efficiently
 - possibly move an object around?
(sokoban?)

Our Robot



What Is Expected From You

- attend the seminars
- bring you own laptop
- do your homeworks
- be proactive (eg. build test arena)
- use VCS and make your sources public so we can inspire & learn from each other

Electronics Preliminaries

Required Level of Knowledge



**DON'T
PANIC**

Only a small subset of high-school physics & common sense is required

Voltage and Current

Voltage

- is a *potential* for current to flow
- denoted as U
- measured in volts (V)
- measured between two points

Waterfall parable:

- voltage is the height, current is the amount of water
- "the power" is linear to the height and the amount


Current flows from positive to negative potential ¹

¹electrons actually go the other way

Current

- is an amount of electrons flowing
- denoted as I
- measured in amperes (A)
- measured on a single point

Voltage and Current

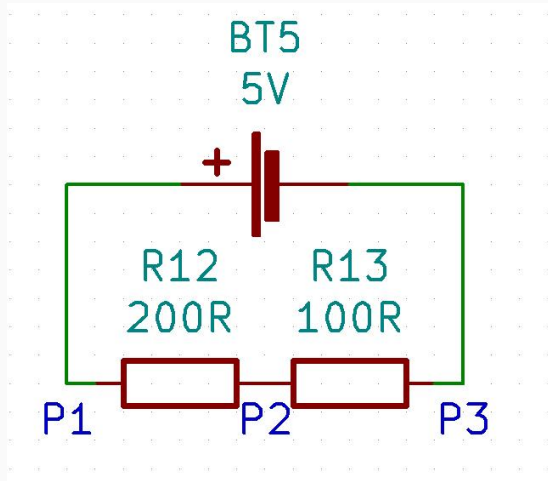


It makes sense to talk about:

- current at point P1
- current at point P2
- current at point P3
- voltage between points P1 and P2
- voltage between points P2 and P3
- voltage between points P1 and P3


Nothing else makes sense.

Resistor

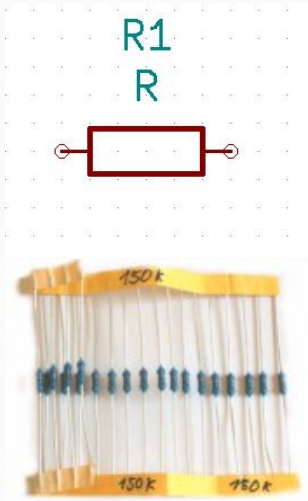

- limits the current flow
- properties:
 - resistance (R), measured in ohms (Ω)
 - maximal power dissipation, measured in watts (W)
- typical usage:
 - limit current (e.g. for LED)
 - divide voltage (pull-up/pull-down)
- notation of the units:
 - $42\ \Omega = 42R$
 - $4200\ \Omega = 4k2$
 - $2500000\ \Omega = 2M5$

Capacitor

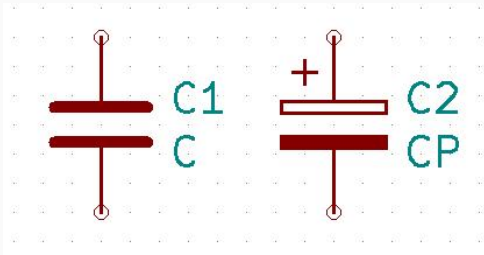

- stores (small amount) of energy
- properties:
 - capacity (C), measured in Farads (F)
 - maximal rated voltage
- typical usage:
 - analog circuitry
 - power filtering
 - oscillators
- notation of the units:
 - $10 \text{ pF} = 10\text{p}$
 - $100 \text{ nF} = 100\text{n}$
 - $4700 \text{ uF} = 4\text{u}7$

Diode


D3

D




D4

LED

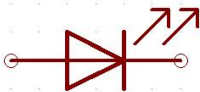


- conducts current only in one direction
- LED – light diode emitting
- properties:
 - forward voltage (V_f)
 - maximal current, (nominal current for LED)
- typical usage:
 - rectification
 - power spike filtering
 - LED – light

Transistor (bipolar)

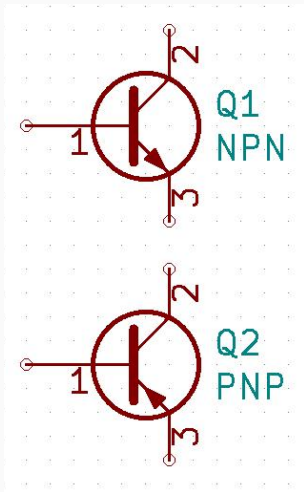

- acts as a valve (small amount of current controls flow)
 - NPN – current going **into** base opens it
 - PNP – current going **from** base opens it
- properties:
 - maximal current
 - amplification (denoted h_{FE})
 - maximal switching frequency
 - maximal power dissipation
- typical usage:
 - power switch
 - basic element of logic gates

Transistor (unipolar)

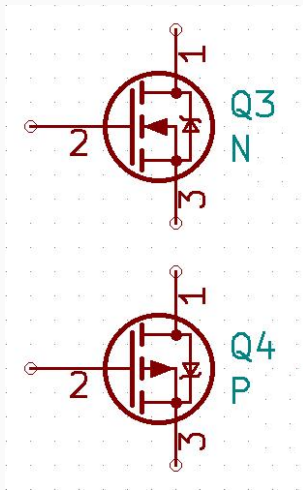

- acts as a valve (voltage controls current flow)
 - N-channel – **positive** voltage between gate and source opens it
 - P-channel – **negative** voltage between gate and source opens it
- properties:
 - maximal current
 - maximal switching frequency
 - maximal power dissipation
 - GS-voltage to current characteristic
 - on-resistance
- typical usage:
 - power switching
 - low-power
- better parameters than bipolar, not so foolproof

"The Formulas" – Ohm's Law, Electric Power & Kirchhoff's Law

Ohms law

$$U = I \cdot R$$

Electric power

$$P = U \cdot I$$


Kirchhoff's law

$$0 = \sum_{k=1}^n I_k, 0 = \sum_{k=1}^m U_k$$

Usage: everywhere


- resistor values
- power losses (thermal dissipation)
- voltage dividers
- etc.

Example – Serial Connection

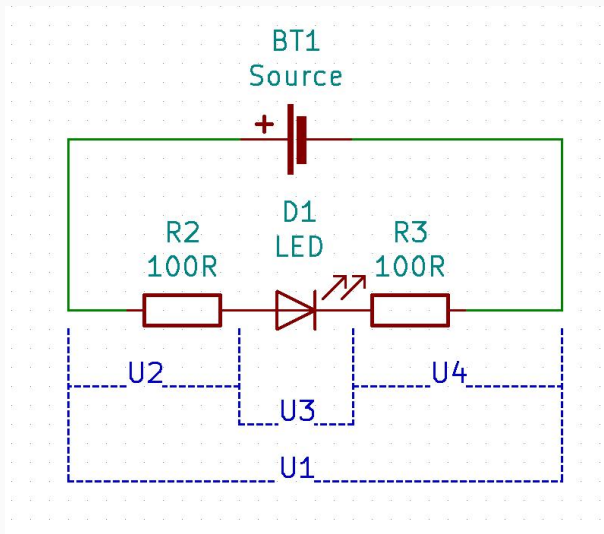


- there is the same current I going through all the points of the circuit
- U_1 is the voltage on the source terminals
- $U_1 = U_2 + U_3 + U_4$

Example – Parallel Connection

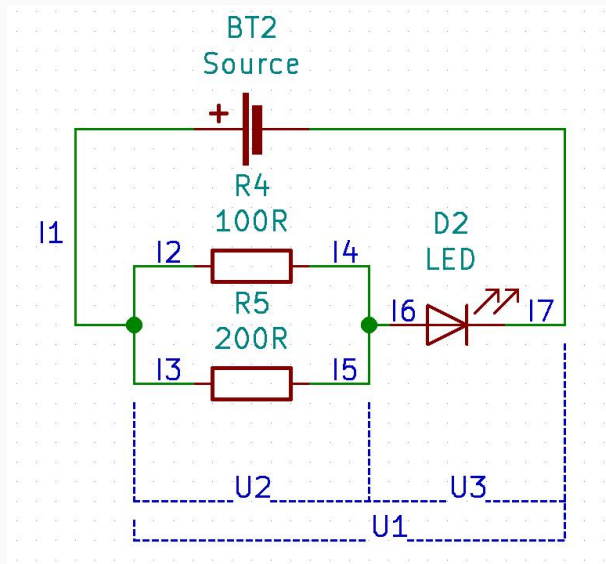


- U_1 is the voltage on the source terminals
- $U_1 = U_2 + U_3$
- $I_1 = I_6 = I_7$
- $I_2 = I_4$
- $I_3 = I_5$
- $I_1 = I_2 + I_3$

HW 1

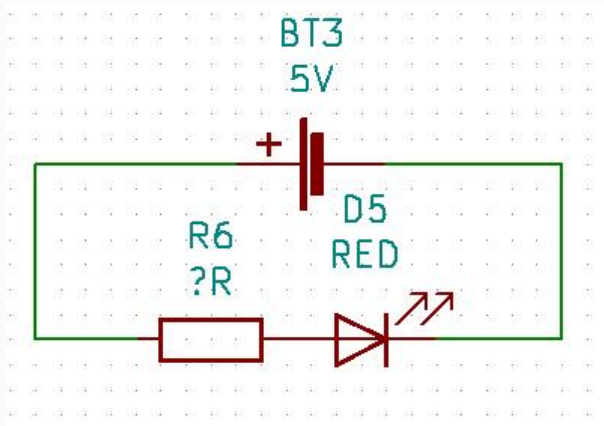

- there is 5V voltage source
- desired current through LED is 10 mA
- forward voltage drop of red LED at 10 mA is 2.2 V
- what is an appropriate value for R6?

HW 2

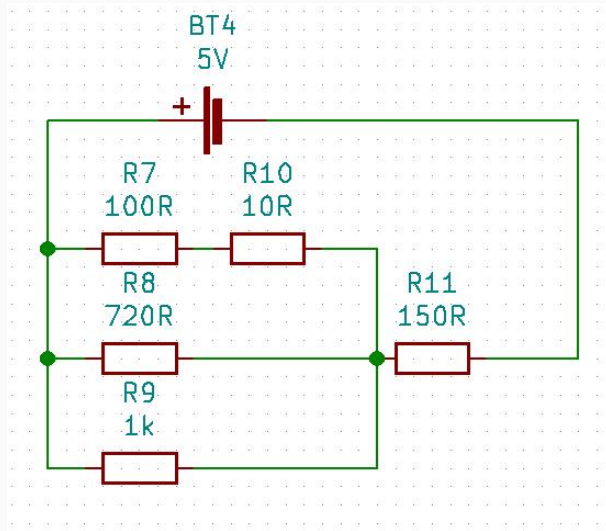

- identify all possible voltages and currents in the circuit
- think about their relations
- determine their values

Prepare the PlatformIO toolchain on your machine for the next lecture.

<https://platformio.org/>



Source: <https://xkcd.com/356/>